



United International University

Dept. of Computer Science & Engineering (CSE)

Trimester: Fall 2022

CSE1326: Digital Logic Design Laboratory

Lab Report-

ID

0	1	1	2	2	1	4	9	4
---	---	---	---	---	---	---	---	---

Name

Mezbah Uddin

Section

Group No

Experiment No

Experiment Name

Arbitrary sequence counter

Date of Performance

				2	0	2	3
--	--	--	--	---	---	---	---

Date of Submission

				2	0	2	3
--	--	--	--	---	---	---	---

Disclaimer:

I hereby certify that this lab report is prepared by me only. I did not copy any part of this from anybody and did not let other copy any part of my report.

Signature of the Teaching Assistant

Signature of the Student

Experiment-01

Step-01:

❖ Instrument:

- use IC's
- use Logism Software
- Use J-k flip flop buildup state table
- Use k-map for equation
- And finally use Logism diagram for create circuit Diagram

❖ Design circuit to count the sequence:



Step-02:

• Format Table:

INPUT		OUTPUT	
Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

• State Table:

NO.	Present State			Next State			Input					
	Q ₂	Q ₁	Q ₀	N ₂	N ₁	N ₀	J ₂	K ₂	J ₁	K ₁	J ₀	K ₀
							Q ₂ \N ₂		Q ₁ \N ₁		Q ₀ \N ₀	
00	0	0	0	0	1	0	0	X	1	X	0	X
01	0	0	1	1	1	0	1	X	1	X	X	1
02	0	1	0	1	1	1	1	X	X	0	1	X
03	0	1	1	0	0	1	0	X	X	1	X	0
04	1	0	0	0	0	0	X	1	0	X	0	X
05	1	0	1	0	1	1	X	1	1	X	X	0
06	1	1	0	0	0	0	X	1	X	1	0	X
07	1	1	1	1	0	1	X	0	X	1	X	0

✚ Step-03:

➤ Use k-map for J_2 :

BC \ A	B'C'	B'c	BC	BC'
A'		1		1
A	X	X	X	X

$$\text{Equation } J_2 = B'C + BC'$$

➤ Use k-map for K_2 :

BC \ A	B'C'	B'c	BC	BC'
A'	X	X	X	X
A	1	1		1

$$\text{Equation } K_2 = B' + C'$$

➤ Use k-map for J_1 :

BC \ A	B'C'	B'c	BC	BC'
A'	1	1	X	X
A		1	x	X

$$\text{Equation } J_1 = C + A'$$

➤ Use k-map for K_1 :

BC		$B'C'$	$B'c$	BC	BC'
A					
A'		X	X	1	
A		X	X	1	1

Equation $K_1 = C + A$

➤ Use k-map for J_0 :

BC		$B'C'$	$B'c$	BC	BC'
A					
A'			X	X	1
A			X	X	

Equation $J_0 = A'B$


➤ Use k-map for K_0 :

BC		$B'C'$	$B'c$	BC	BC'
A					
A'		X	1		X
A		X			X

Equation $K_0 = A'B'$

Step-04:

● **Circuit Diagram:**

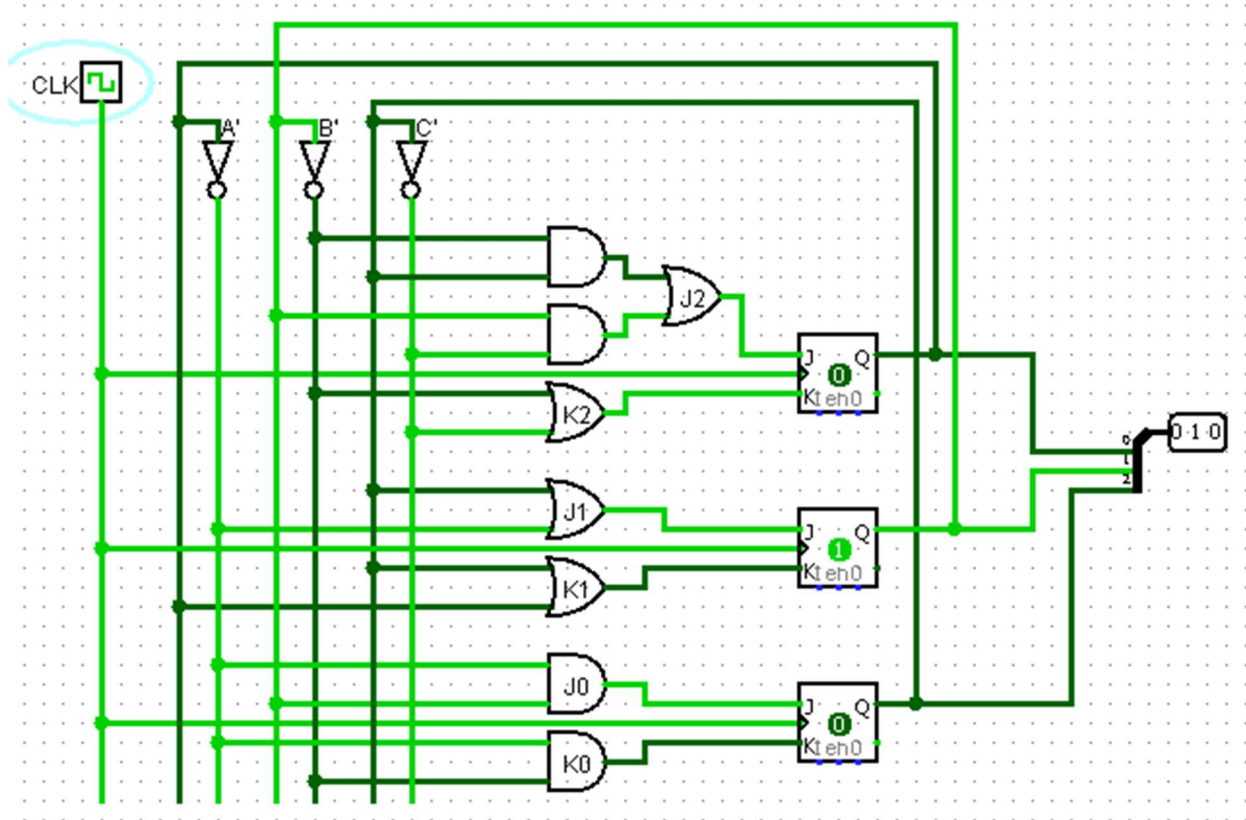

END